

# AIG to CNF



## » Most modern SAT solvers accept input formulae in conjunctive normal form (CNF)

- > Literals: variables & their complements, e.g.  $a, b, \neg c$
- > Clauses: disjunction of literals, e.g.  $(a \vee b \vee \neg c)$
- > Cubes: conjunction of literals, e.g.  $(a \wedge b \wedge \neg c)$
- > CNF formula: conjunction of clauses, product-of-sums  
e.g.  $(a \vee b \vee \neg c) \wedge (\neg a \vee \neg b \vee d)$
- > DNF formula: disjunction of cubes, sum-of-products  
e.g.  $(a \wedge c \wedge \neg d) \vee (\neg b \wedge d \wedge c)$

## » Given AIG for $f$ , generating $f$ in CNF can blow up badly

- > Start from DNF formula  $f$  (size:  $|f|$ )
- > Build AIG for  $f$  (size:  $O(|f|)$ )
- > Convert AIG to CNF
  - + Effectively convert DNF to CNF: known worst-case exponential blow-up

# AIG to CNF




- » **Solution:** Given AIG for  $f$ , generate **equisatisfiable**  $g$  in CNF
- » **Equisatisfiability**
  - >  $f$  and  $g$  equisatisfiable iff **both  $f$  and  $g$  are satisfiable** or **both are unsatisfiable**
  - >  $(a \vee b)$  equisatisfiable with  $(c \wedge d)$ , not equisatisfiable with  $d \wedge (\neg d \vee c) \wedge \neg c$
  - > Checking satisfiability of  $g$  tells us if  $f$  is satisfiable
- » **Tseitin encoding**
  - > Given a Boolean circuit (AIG is a special case) for  $f$ , generate equisatisfiable  $g$ 
    - +  $g$  is in CNF
    - + Every satisfying assignment for  $f$  gives unique satisfying assignment for  $g$  and vice-versa
    - + Size of  $g$  linear in size of circuit (AIG) for  $f$
  - > Widely used in SAT solving context

# AIG to CNF: Tseitin Encoding


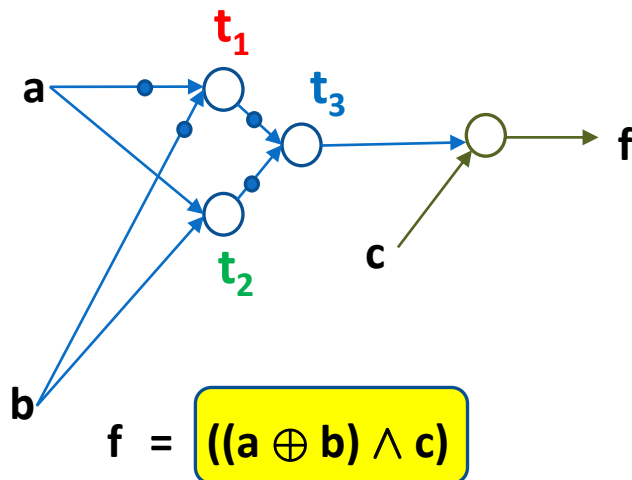
## » Given Boolean circuit (or AIG) for $f$

- > Associate new variable with output of each gate
- > For each Boolean gate, generate formula expressing output in terms of inputs
- > Convert each formula generated above to CNF
  - + Boolean gate with fixed # inputs  $\Rightarrow$  CNF formula for gate is of fixed size
- > Conjoin CNF formula for each gate and output variable of circuit



$$t_1 \leftrightarrow (\neg a \wedge \neg b)$$


$$t_2 \leftrightarrow (a \wedge b)$$

$$t_3 \leftrightarrow (\neg t_1 \wedge \neg t_2)$$

$$f \leftrightarrow (t_3 \wedge c)$$

$$\begin{aligned} &(\neg t_1 \vee \neg a) \wedge (\neg t_1 \vee \neg b) \wedge \\ &(a \vee b \vee t_1) \quad \wedge \\ &(\neg t_2 \vee a) \wedge (\neg t_2 \vee b) \wedge \\ &(\neg a \vee \neg b \vee t_2) \quad \wedge \\ &(\neg t_3 \vee \neg t_1) \wedge (\neg t_3 \vee \neg t_2) \wedge \\ &(t_1 \vee t_2 \vee t_3) \quad \wedge \\ &(\neg f \vee t_3) \wedge (\neg f \vee c) \wedge \\ &(\neg t_3 \vee \neg c \vee f) \quad \wedge f \end{aligned}$$

# AIG To CNF: Tseitin Encoding

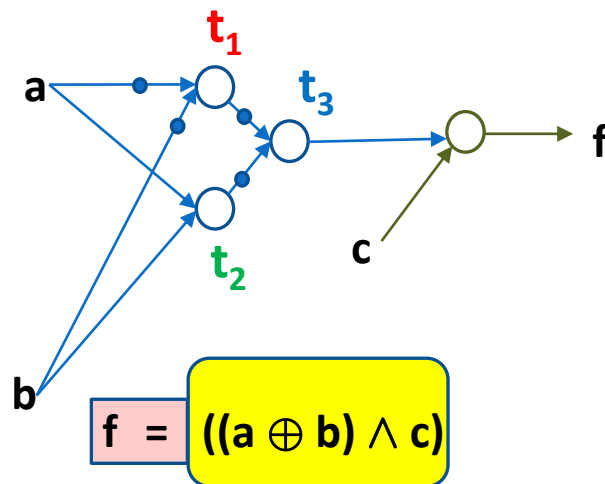

$$t_1 \leftrightarrow (\neg a \wedge \neg b)$$

$$t_2 \leftrightarrow (a \wedge b)$$

$$t_3 \leftrightarrow (\neg t_1 \wedge \neg t_2)$$

$$f \leftrightarrow (t_3 \wedge c)$$

$$(\neg t_1 \vee \neg a) \wedge (\neg t_1 \vee \neg b) \wedge (a \vee b \vee t_1)$$

$$(\neg t_2 \vee a) \wedge (\neg t_2 \vee b) \wedge (\neg a \vee \neg b \vee t_2)$$

$$(\neg t_3 \vee \neg t_1) \wedge (\neg t_3 \vee \neg t_2) \wedge (t_1 \vee t_2 \vee t_3)$$

$$(\neg f \vee t_3) \wedge (\neg f \vee c) \wedge (\neg t_3 \vee \neg c \vee f)$$

= g

## » Bijection between SAT assignments of f and g

For every SAT assignment of f

> Evaluate all gate outputs for given assignment of inputs

> a = 1, b = 0, c = 1 gives a = 1, b = 0, c = 1, t<sub>1</sub> = 0, t<sub>2</sub> = 0, t<sub>3</sub> = 1, f = 1

For every SAT assignment of g

> Project assignment on variables of f

> a = 1, b = 0, c = 1, t<sub>1</sub> = 0, t<sub>2</sub> = 0, t<sub>3</sub> = 1, f = 1 gives a = 1, b = 0, c = 1

SAT assignment of g

SAT assignment of f