





Chapter 4

Combinational Logic



Outline

- **Combinational Circuits**
- Analysis and Design Procedures
- Binary Adders
- Other Arithmetic Circuits
- Decoders and Encoders
- Multiplexers



Combinational v.s Sequential Circuits

- Logic circuits may be ***combinational*** or ***sequential***
- Combinational circuits:
 - Consist of ***logic gates*** only
 - Outputs are determined from the present values of inputs
 - Operations can be specified by a set of Boolean functions
- Sequential circuits:
 - Consist of ***logic gates*** and ***storage elements***
 - Outputs are a function of the inputs and the state of the storage elements
 - Depend not only on present inputs, but also on past values
 - Circuit behavior must be specified by a time sequence of inputs and internal states

Combinational Circuit (1/2)

- A combinational circuit consists of
 - Input variables
 - Logic gates
 - Output variables

 




Fig. 4-1 Block Diagram of Combinational Circuit



Combinational Circuit (2/2)

- Each input and output variable is a binary signal
 - Represent logic 1 and logic 0
- There are 2^n possible binary input combinations for n input variable
- Only one possible output value for each possible input combination
- Can be specified with a truth table
- Can also be described by m Boolean functions, one for each output variable
 - Each output function is expressed in terms of n input variables



Outline

- Combinational Circuits
- Analysis and Design Procedures
- Binary Adders
- Other Arithmetic Circuits
- Decoders and Encoders
- Multiplexers




Analysis Procedure

- Analysis: determine the function that the circuit implements
 - Often start with a given logic diagram
- The analysis can be performed by
 - Manually finding Boolean functions
 - Manually finding truth table
 - Using a computer simulation program
- First step: make sure that circuit is combinational
 - Without feedback paths or memory elements
- Second step: obtain the output Boolean functions or the truth table

Output Boolean Functions (1/3)

Step 1:

 - Label all gate outputs that are a function of input variables
- Determine Boolean functions for each gate output




$$\begin{aligned} F_2 &= AB + AC + BC \\ T_1 &= A + B + C \\ T_2 &= ABC \end{aligned}$$

Output Boolean Functions (2/3)

Step 2:

 - Label the gates that are a function of input variables and previously labeled gates
- Find the Boolean function for these gates




$$\begin{aligned} T_3 &= F'_2 T_1 \\ F_1 &= T_3 + T_2 \end{aligned}$$

Output Boolean Functions (3/3)

Step 3:

- Obtain the output Boolean function in term of input variables
 - By repeated substitution of previously defined functions

$$\begin{aligned}F_1 &= T_3 + T_2 = F'_2 T_1 + ABC \\&= (AB + AC + BC)' (A + B + C) + ABC \\&= (A' + B')(A' + C')(B' + C')(A + B + C) + ABC \\&= (A' + B' C')(AB' + AC' + BC' + B' C) + ABC \\&= A' BC' + A' B' C + AB' C' + ABC\end{aligned}$$



Truth Table

- To obtain the truth table from the logic diagram:
 1. Determine the number of input variables
For n inputs:
 - 2^n possible combinations
 - List the binary numbers from 0 to $2^n - 1$ in a table
 2. Label the outputs of selected gates
 3. Obtain the truth table for the outputs of those gates that are a function of the input variables only
 4. Obtain the truth table for those gates that are a function of previously defined variables at step 3
 - Repeatedly until all outputs are determined

Truth Table for Fig. 4-2

A	B	C	F ₂	F ₂	T ₁	T ₂	T ₃	F ₁
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1



Design Procedure

- Design procedure:
 - Input: the specification of the problem
 - Output: the logic circuit diagram (or Boolean functions)
- Step 1: determine the required number of inputs and outputs from the specification
- Step 2: derive the truth table that defines the required relationship between inputs and outputs
- Step 3: obtain the simplified Boolean function for each output as a function of the input variables
- Step 4: draw the logic diagram and verify the correctness of the design

Code Conversion Example

- Convert from BCD code to Excess-3 code
- The 6 input combinations not listed are don't cares
- These values have no meaning in BCD
- We can arbitrary assign them to 1 or 0

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

Maps for Code Converter (1/2)

- The six don't care minterms (10~15) are marked with X

		CD		C	
		00	01	11	10
A	00	1			1
	01	1			1
	11	X	X	X	X
	10	1		X	X
		D			
		$z = D'$			

		CD		C	
		00	01	11	10
A	00	1		1	
	01	1		1	
	11	X	X	X	X
	10	1		X	X
		D			
		$y = CD + C'D'$			

Maps for Code Converter (2/2)

		<i>CD</i>		<i>C</i>	
<i>AB</i>		00	01	11	10
<i>A</i>	00		1	1	1
	01	1			
	11	X	X	X	X
	10		1	X	X

D

B

$$X = B'C + B'D + BC'D'$$

		<i>CD</i>		<i>C</i>	
<i>AB</i>		00	01	11	10
<i>A</i>	00				
	01		1	1	1
	11	X	X	X	X
	10	1	1	X	X

D

B

$$w = A + BC + BD$$

Logic Diagram for the Converter

- There are various possibilities for a logic diagram that implements a circuit
- A two-level logic diagram may be obtained directly from the Boolean expressions derived by the maps
- The expressions may be manipulated algebraically to use common gates for two or more outputs
 - Reduce the number of gates used


$$z = D'$$

$$y = CD + C' D' = CD + (C + D)'$$


$$\begin{aligned} x &= B'C + B'D + BC' D' = B' (C + D) + BC' D' \\ &= B' (C + D) + B(C + D)' \end{aligned}$$

$$w = A + BC + BD = A + B(C + D)$$

Logic Diagram for the Converter

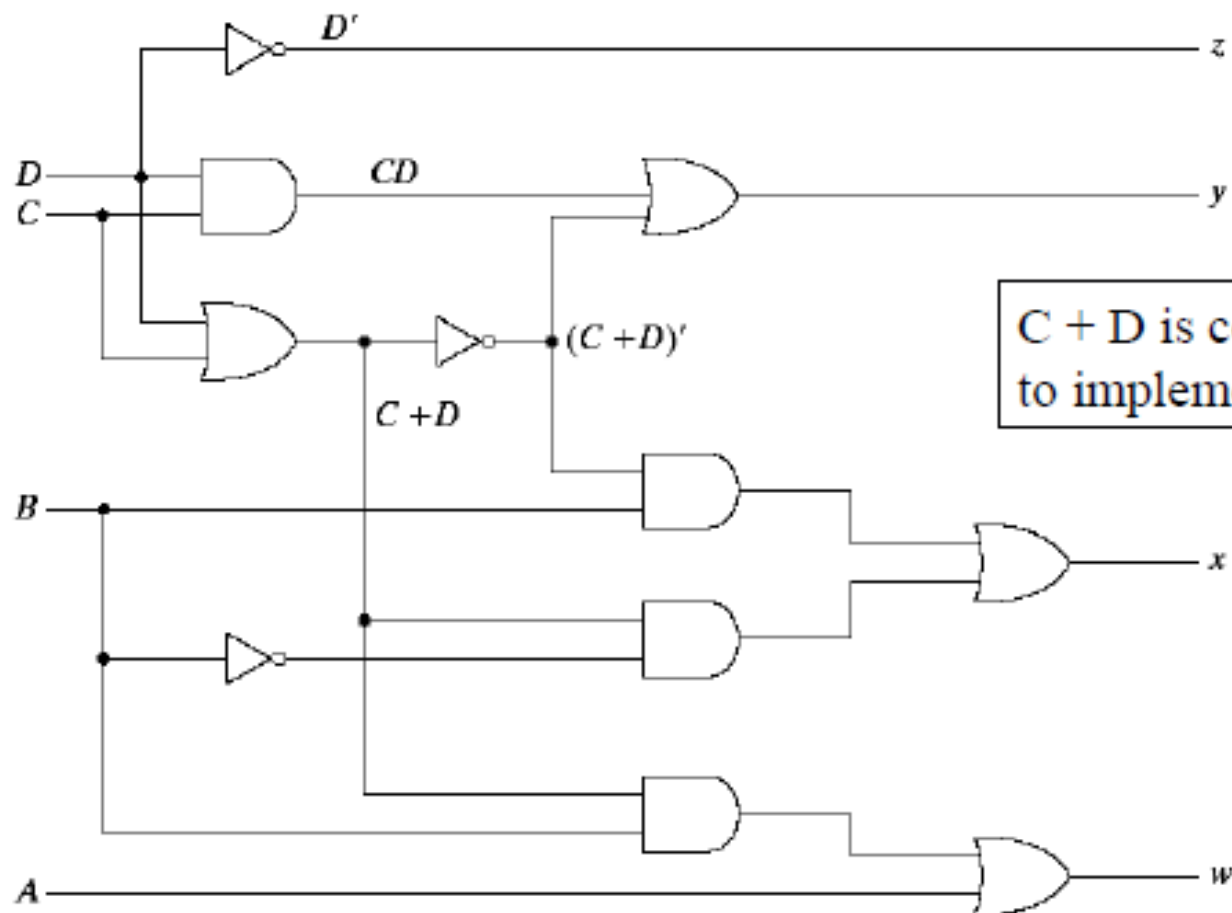


$C + D$ is commonly used
to implement the three outputs



Outline

- Combinational Circuits
- Analysis and Design Procedures
- Binary Adders
- Other Arithmetic Circuits
- Decoders and Encoders
- Multiplexers



Adder

- The most basic arithmetic operation is the addition of two binary digits
 - When both augend and addend bits are equal to 1, the binary sum consists of two digits ($1 + 1 = 10$)
 - The higher significant bit of this result is called a ***carry***
- A combination circuit that performs the addition of two bits is ***half adder***
- An adder performs the addition of 2 significant bits and a previous carry is called a ***full adder***

Half Adder


- Half adder
 - Inputs: x and y
 - Outputs: S (for sum) and C (for carry)

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


$$S = x'y + xy'$$

$$C = xy$$

Implementation of a Half Adder

 
 
$$\begin{aligned} \text{(a)} \quad S &= xy' + x'y \\ C &= xy \end{aligned}$$



$$\begin{aligned} \text{(b)} \quad S &= x \oplus y \\ C &= xy \end{aligned}$$

Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

x, y: the two significant bits to be added
 z: the carry from the previous position


		yz		y	
		00	01	11	10
x	0		1		1
x	1	1		1	

$$S = x'y'z + x'yz' + xy'z' + xyz$$


		yz		y	
		00	01	11	10
x	0			1	
x	1		1	1	1

$$\begin{aligned} C &= xy + xz + yz \\ &= xy + xy'z + x'yz \end{aligned}$$

Implementation of a Full Adder

 

 
$$S = x' y' z + x' y z' + x y' z' + x y z$$



$$C = xy + xz + yz$$

Implementation of a Full Adder

 - A full adder can be implemented with two half adders and an OR gate




$$\begin{aligned}
 S &= z \oplus (x \oplus y) \\
 &= z'(xy' + x'y) + z(xy' + x'y)' \\
 &= z'(xy' + x'y) + z(xy + x'y') \\
 &= xy'z' + x'yz' + xyz + x'y'z
 \end{aligned}$$

$$\begin{aligned}
 C &= z(xy' + x'y) + xy \\
 &= xy'z + x'yz + xy \\
 &= xy'z + x'yz + xyz + xyz' \\
 &= xz + yz + xy
 \end{aligned}$$

Binary Adder

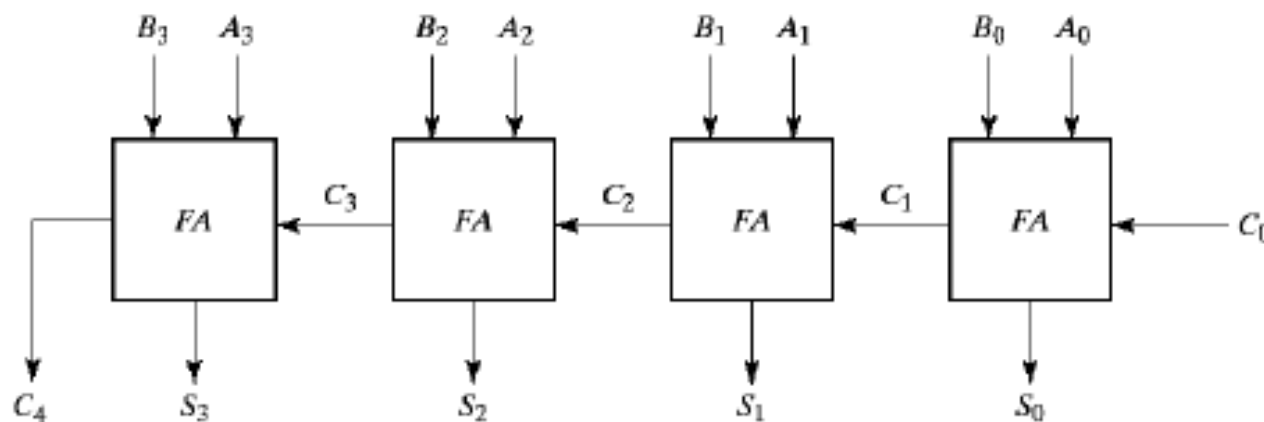- A binary adder produces the arithmetic sum of two binary numbers
- Can be constructed with full adders connected in cascade
 - The output carry from each full adder is connected to input carry of the next full adder in the chain
 - n-bit binary *ripple carry adder* is connected by n FAs



4-bit Adder Example

- Consider two binary number $A = 1011$ and $B = 0011$

Subscript i :	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

RTL for full adder

```
library ieee;
use ieee.std_logic_1164.all;

entity andGate is
    port A, B : in std_logic;
         F : out std_logic;
end andGate;

architecture func of andGate is
begin
    F <= A and B;
end func;
--=====

--Here we define the XOR gate that we need for
--the Half Adder
library ieee;
use ieee.std_logic_1164.all;

entity xorGate is
    port A, B : in std_logic;
         F : out std_logic;
end xorGate;

architecture func of xorGate is
begin
    F <= A xor B;
end func;
--=====

-- At this point we construct the half adder
-- using the AND and XOR gates
library ieee;
use ieee.std_logic_1164.all;

entity halfAdder is
    port A, B : in std_logic;
        sum, Cout : out std_logic;
end halfAdder;

architecture halfAdder of halfAdder is
    component andGate is -- import AND Gate
        port A, B : in std_logic;
             F : out std_logic;
        end component;

    component xorGate is -- import XOR Gate
        port A, B : in std_logic;
             F : out std_logic;
        end component;

begin
    G1 : andGate port map(A, B, sum);
    G2 : xorGate port map(A, B, Cout);
end halfAdder;
--===== END HALF ADDER

-- Now we define the OR gate that we need for the Full Adder
library ieee;
use ieee.std_logic_1164.all;

entity orGate is
    port A, B : in std_logic;
         F : out std_logic;
end orGate;

architecture func of orGate is
begin
    F <= A or B;
end func;
--=====

-- We are finally ready to build the Full Adder
library ieee;
use ieee.std_logic_1164.all;


entity fullAdder is
    port A, B, Cin : in std_logic;
        sum, Cout : out std_logic;
end fullAdder;

architecture fullAdder of fullAdder is
    component halfAdder is -- import Half Adder entity
        port A, B : in std_logic;
             sum, Cout : out std_logic;
        end component;

    component orGate is -- import OR Gate entity
        port A, B : in std_logic;
             F : out std_logic;
        end component;

    signal half0half, half0Or1, half0Or2 : std_logic;

begin
    G1 : halfAdder port map(A, B, half0half, half0Or1);
    G2 : halfAdder port map(half0half, Cin, sum, half0Or2);
    G3 : orGate port map(half0Or1, half0Or2, Cout);
end fullAdder;
--=====
END
```





Carry Propagation

- As in a combinational circuit, the signal must propagate through the gates before the correct output sum is available in the output terminals
- The total propagation time is equal to the propagation delay of a typical gate times the number of levels in the circuit
- The longest propagation delay in an adder is the time that carry propagates through the full adders
- Each bit of the sum output depends on the value of the input carry
 - The value of S_i will be in final value only after the input carry C_i has been propagated

Full Adder with P and G

 - The full adder can be redrawn with two internal signals P (propagation) and G (generation)
- The signal from input carry C_i to output carry C_{i+1} propagates through an AND and a OR gate (2 gate levels)
 - For n-bit adder, there are $2n$ gate levels for the carry to propagate from input to output






Carry Propagation

- The ***carry propagation time*** is a limiting factor on the speed with which two numbers are added
- All other arithmetic operations are implemented by successive additions
 - The time consumed during the addition is very critical
- To reduce the carry propagation delay
 - Employ faster gates with reduced delays
 - Increase the equipment complexity
- Several techniques for reducing the carry propagation time in a parallel adder
 - The most widely used technique employs the principle of ***carry lookahead***

Carry Propagation & Generation

 


carry propagate : $P_i = A_i \oplus B_i$

carry generate : $G_i = A_i B_i$

$S_i = P_i \oplus C_i$

$C_{i+1} = G_i + P_i C_i$

Carry Lookahead Generator

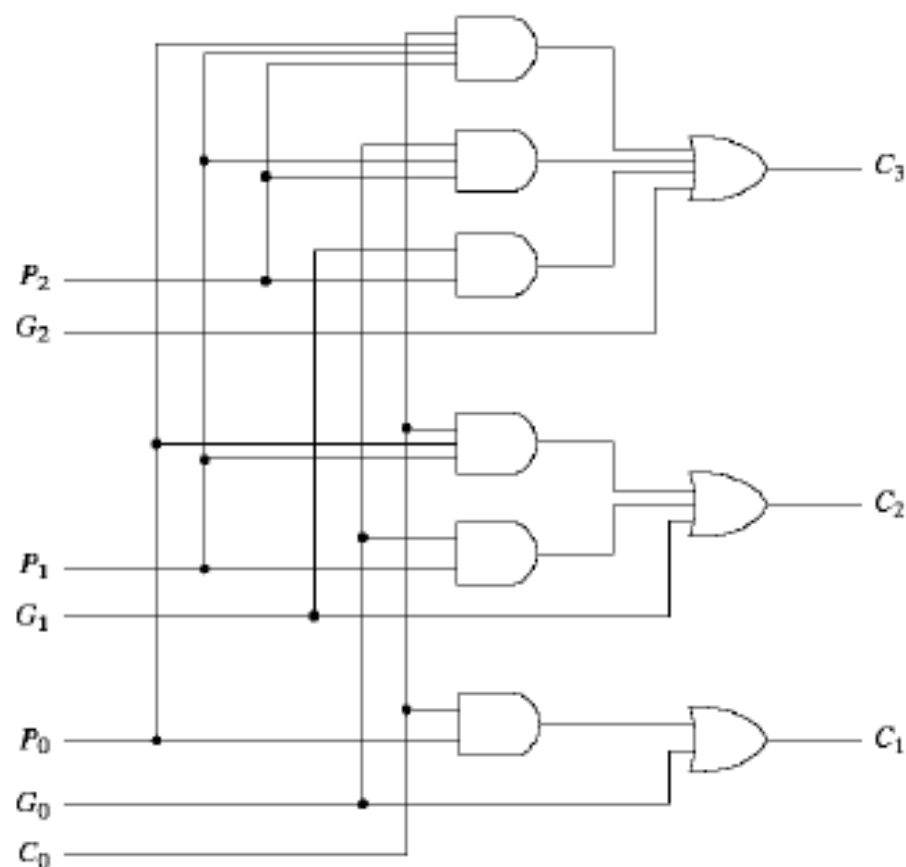

C_0 = input carry

$$C_1 = G_0 + P_0C_0$$

$$C_2 = G_1 + P_1C_1$$


$$= G_1 + P_1(G_0 + P_0C_0)$$

$$= G_1 + P_1G_0 + P_1P_0C_0$$


$$C_3 = G_2 + P_2C_2$$

$$= G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0$$

Carry Lookahead Adder

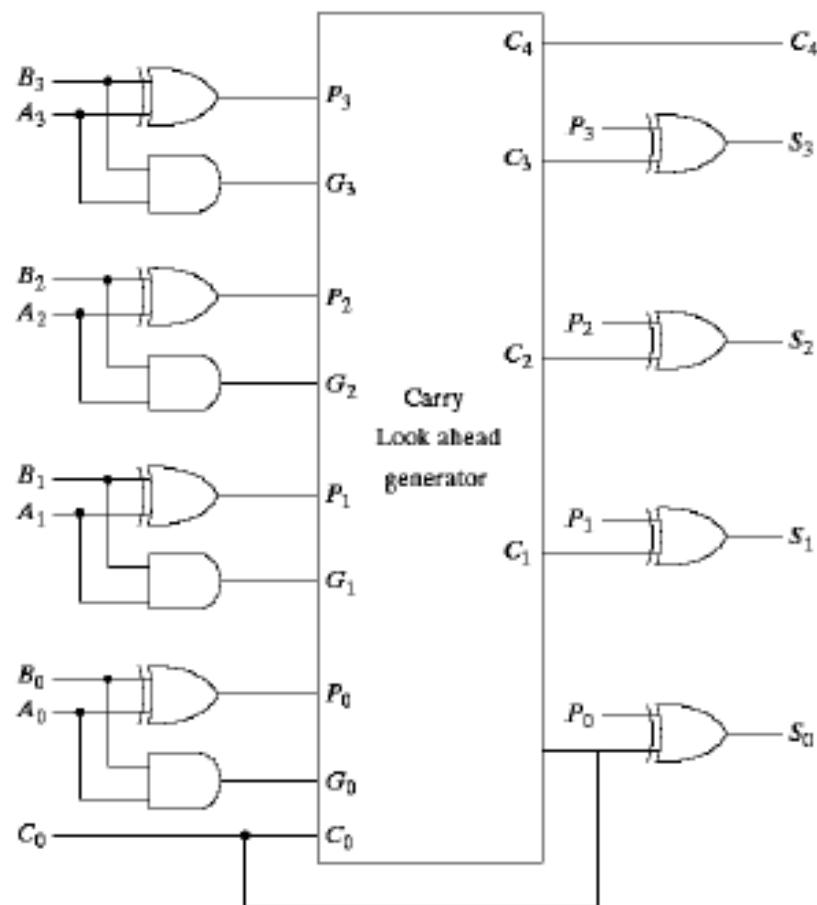


- All output carries are generated after a delay through two levels of gates
- Output S_1 to S_3 can have equal propagation delay times



Outline

- Combinational Circuits
- Analysis and Design Procedures
- Binary Adders
- Other Arithmetic Circuits
- Decoders and Encoders
- Multiplexers




Binary Subtractor

- $A - B$ can be done by taking the 2's complement of B and adding it to A ---> $A - B = A + (-B)$
 - 2's complement can be obtained by taking the 1's complement and adding on to the least significant pair of bits
 - $A - B = A + (B' + 1)$
- The circuit for subtraction $A - B$ consists of an adder with inverter placed between each data input B and the corresponding input of the full adder
- The input carry C_0 must be equal to 1

4-bit Adder-Subtractor

- $M=0$ (Adder)
 - Input of FA is A and B ($B \oplus 0 = B$), and C_0 is 0
- $M=1$ (Subtractor)
 - Input of FA is A and B' ($B \oplus 1 = B'$), and C_0 is 1

x	y	$x \oplus y$	
0	0	0	y
0	1	1	
<hr/>			y'
1	0	1	
1	1	0	

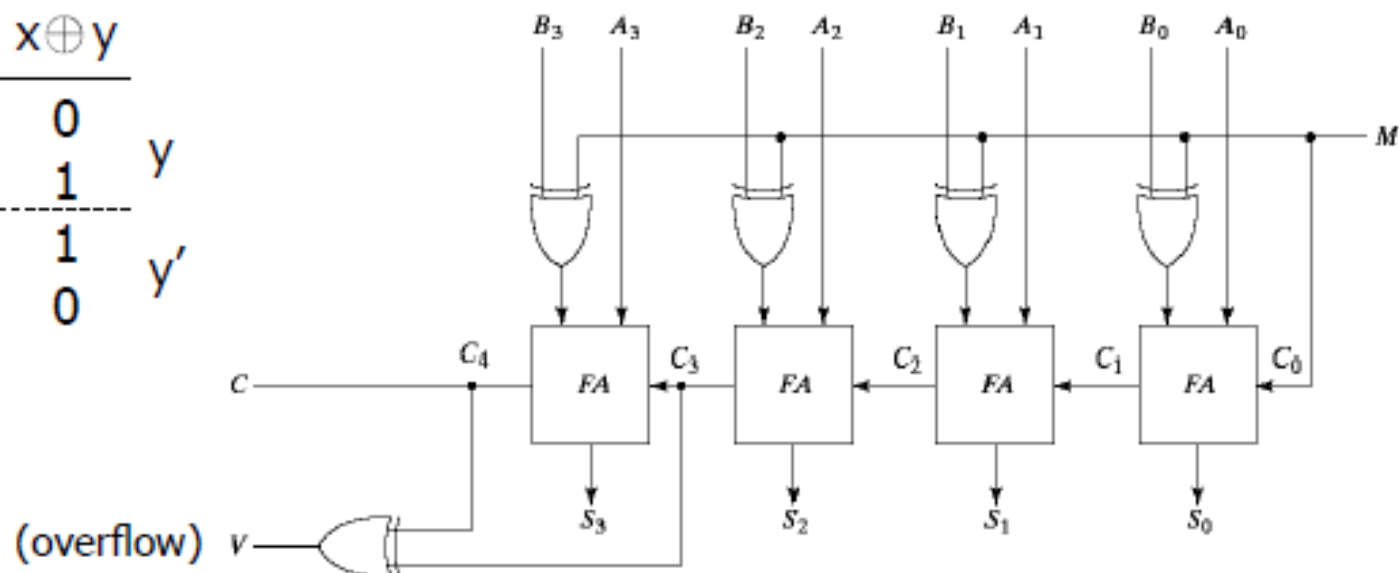





Overflow

- An overflow occurs when two number of n digits each are added and the sum occupies $n+1$ digits
- When two unsigned numbers are added, an overflow is detected from the end carry out of the most significant position
- When two signed numbers are added, the sign bit is treated as part of the number and the end carry does not indicate an overflow
 - Extra overflow detection circuits are required
- An overflow can only occur when two numbers added are ***both positive*** or ***both negative***

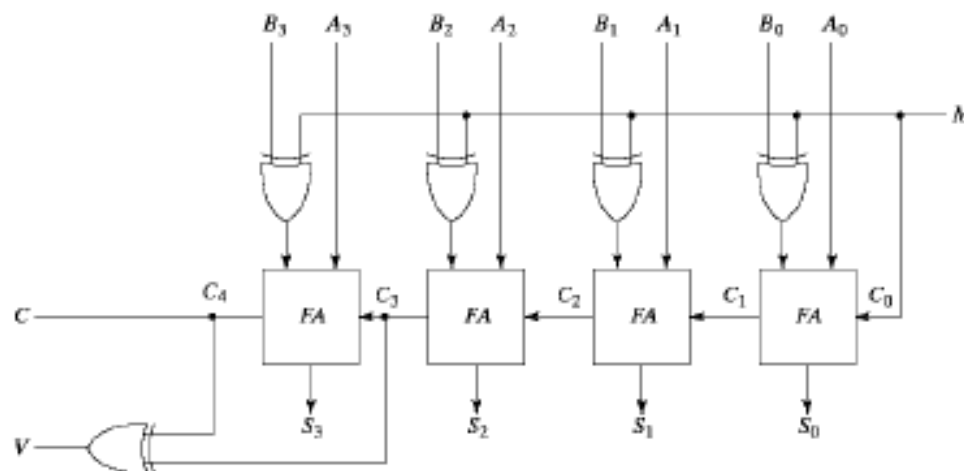- Unsigned
 - C bit detects a *carry* after addition or a *borrow* after subtraction
- Signed
 - V bit detects an overflow
0: no overflow; 1: overflow





Decimal Adder

- A decimal adder requires a minimum of 9 inputs and 5 outputs
 - 1 digit requires 4-bit
 - Input: 2 digits + 1-bit carry
 - Output: 1 digit + 1-bit carry
- BCD adder
 - Perform the addition of two decimal digits in BCD, together with an input carry from a previous stage
 - The output sum cannot be greater than 19 ($9+9+1$)

Derivation of BCD Adder

Binary Sum					BCD Sum					Decimal
K	Z ₈	Z ₄	Z ₂	Z ₁	C	S ₈	S ₄	S ₂	S ₁	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
.....				
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19


BCD Adder

- When the binary sum is equal to or less than 1001_b
 - BCD Sum = Binary Sum
 - $C = 0$
- When the binary sum is greater than 1001_b
 - BCD Sum = Binary Sum + 0110_b
 - $C = 1$

Z_8Z_4 Z_2Z_1		Z_8Z_4			
		00	01	11	10
00				1	
01				1	
11				1	1
10				1	1

$$C = K + Z_8Z_4 + Z_8Z_2$$


Block Diagram of a BCD Adder

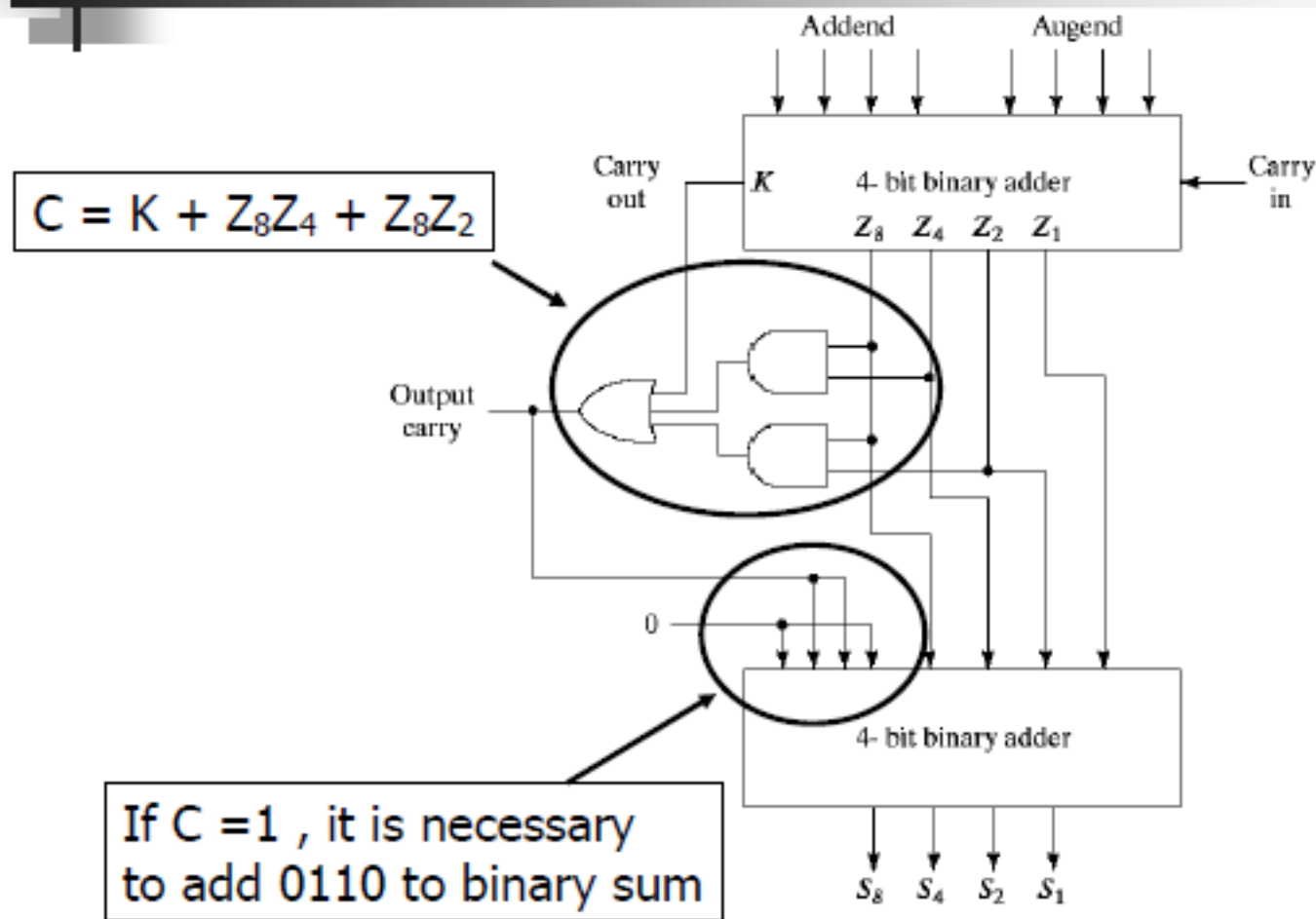



Binary Multiplier

$$\begin{array}{r}
 \begin{array}{cc}
 B_1 & B_0 \\
 A_1 & A_0 \\
 \hline
 A_0 B_1 & A_0 B_0 \\
 A_1 B_1 & A_1 B_0 \\
 \hline
 C_3 & C_2 & C_1 & C_0
 \end{array}
 \end{array}$$

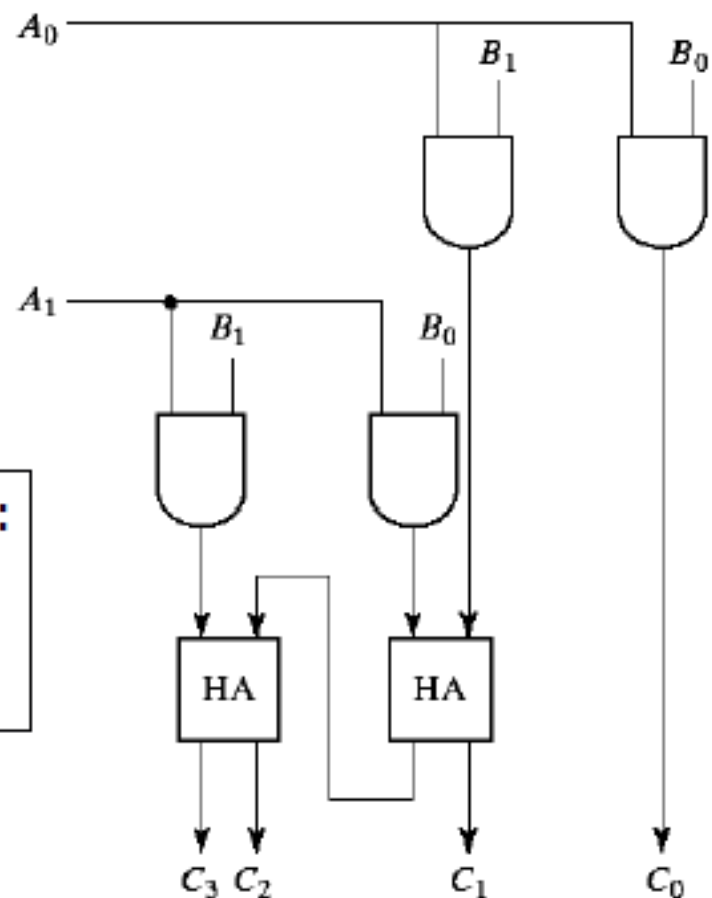For a $J \times K$ bits multiplier, we need:
 $(J \times K)$ AND gates
 $(J - 1)$ K-bit adders
to produce a product of $J+K$ bits



4-Bit By 3-Bit Binary Multiplier

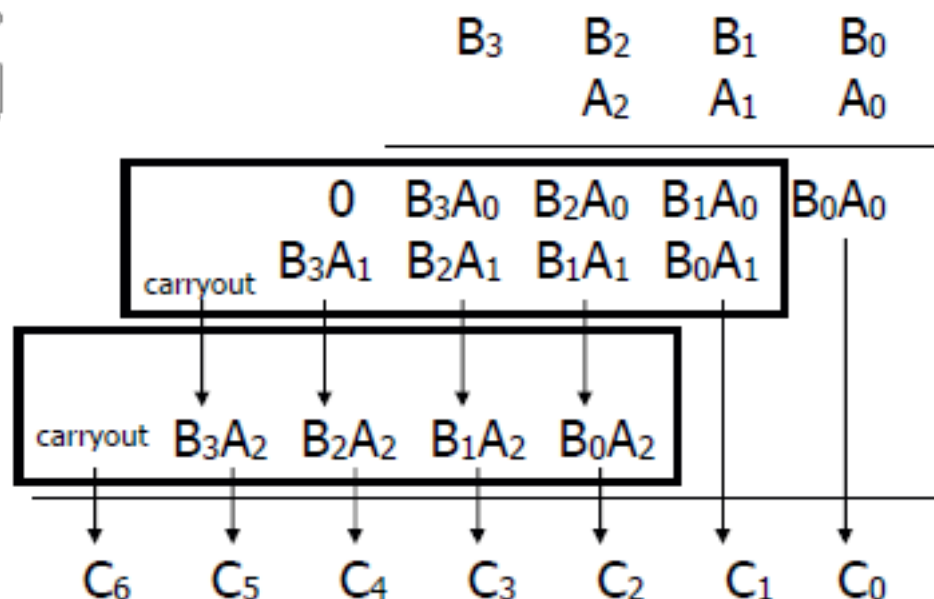 

We need 12 AND gates and two 4-bit adders to produce a product of 7 bits

Magnitude Comparator

- Equal ($A = B$)

- $A_3=B_3$ and $A_2=B_2$ and $A_1=B_1$ and $A_0=B_0$

$$X_i = A_i B_i + A_i' B_i' \text{ for } i = 0, 1, 2, 3$$

$X_i = 1$ means
 A_i and B_i are equal !!

- $(A=B) = X_3 X_2 X_1 X_0$


- Greater ($A > B$) or Less ($A < B$)


- Comparison start from the MSB
- If the two digits are equal, compare the next lower digits
- Continues until a pair of unequal digits is reached
 - A is 1 and B is 0 $\Rightarrow A > B$
 - A is 0 and B is 1 $\Rightarrow A < B$

$$(A > B) = A_3 B_3' + X_3 A_2 B_2' + X_3 X_2 A_1 B_1' + X_3 X_2 X_1 A_0 B_0'$$

$$(A < B) = A_3' B_3 + X_3 A_2' B_2 + X_3 X_2 A_1' B_1 + X_3 X_2 X_1 A_0' B_0$$

4-Bit Magnitude Comparator

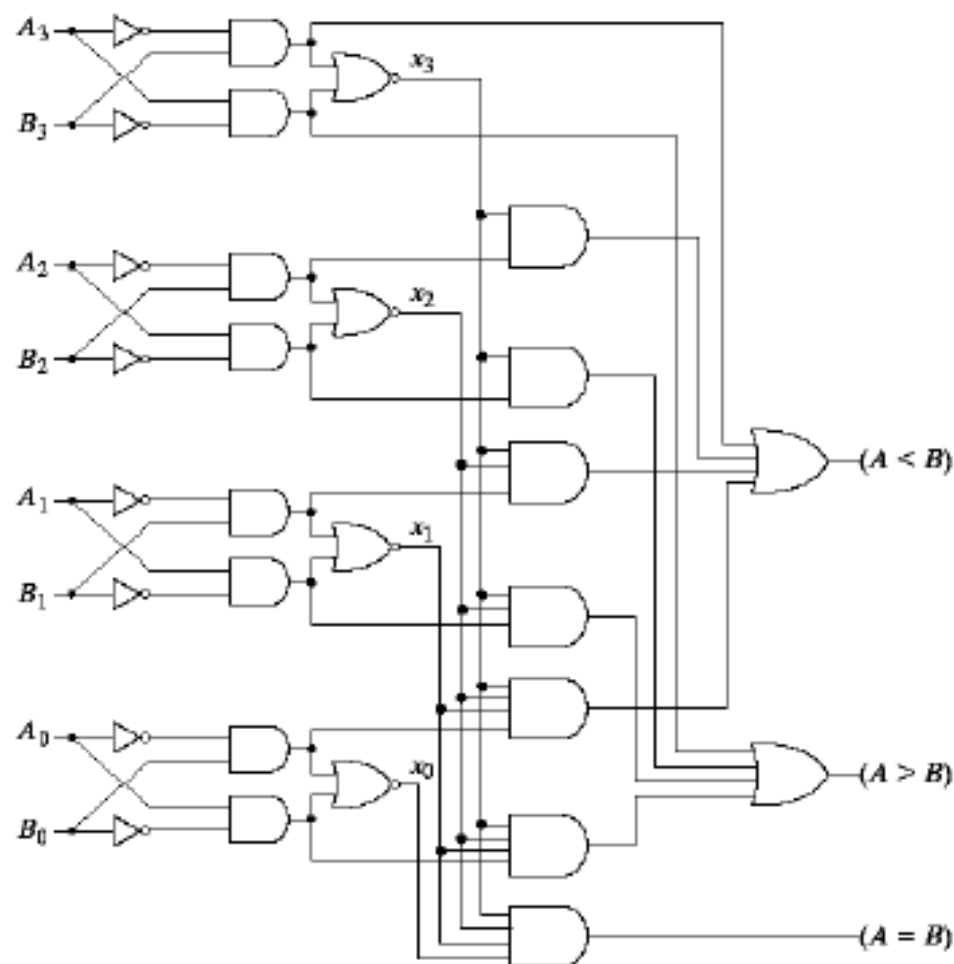



Outline

- Combinational Circuits
- Analysis and Design Procedures
- Binary Adders
- Other Arithmetic Circuits
- Decoders and Encoders
- Multiplexers




Decoder

- A circuit that converts binary information from n input lines to a maximum of 2^n unique output lines
 - May have fewer than 2^n outputs
- A n -to- m -line decoder ($m \leq 2^n$):
 - Generate the m minterms of n input variables
- For each possible input combination, there is only one output that is equal to 1
 - The output whose value is equal to 1 represents the minterm equivalent of the binary number presently available in the input lines

3-to-8-Line Decoder

 
- The 3 inputs are decoded into 8 outputs
- Each represent one of the minterms of the inputs variables



Inputs			Outputs							
x	y	z	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

2-to-4-Line Decoder with Enable

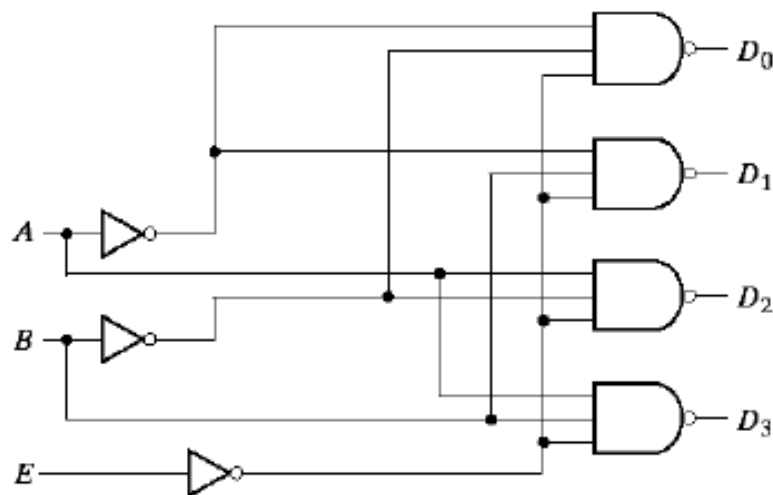
- Some decoders are constructed with NAND gates
 - Generate minterms in their complement form
- An **enable** input can be added to control the operation
 - E=1: disabled
 - None of the outputs are equal to 0



<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃
1	<i>X</i>	<i>X</i>	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

Demultiplexer

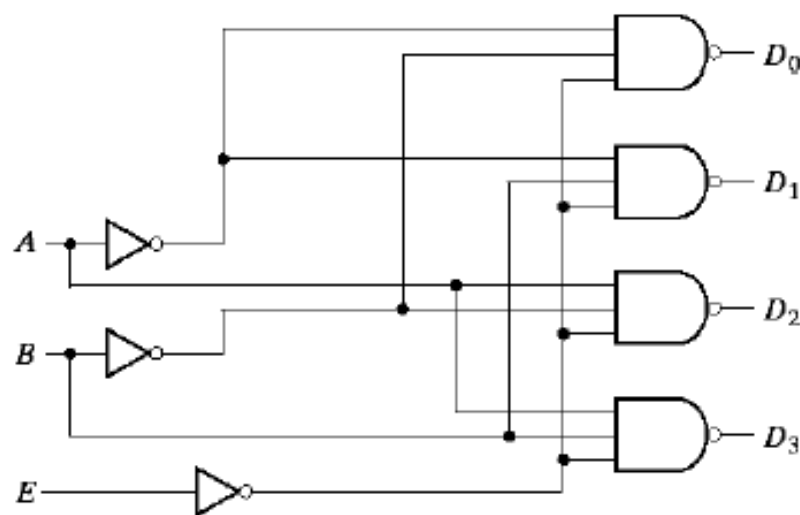- A circuit that receives information from a single line and directs it to one of 2^n possible output lines
- A decoder with enable input can function as a demultiplexer
 - Often referred to as a ***decoder/demultiplexer***



selection			data input			
E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

RTL for decoder (3:8)

```
• -----  
--  
-- Title      : decoder3_8  
-- Design     : vhdl_test  
--  
-----  
--  
-- File       : 3 : 8 Decoder using when else.vhd  
  
library IEEE;  
use IEEE.STD_LOGIC_VECTOR.all;  
  
entity decoder3_8 is  
    port(  
        din : in STD_LOGIC_VECTOR(2 downto 0);  
        dout : out STD_LOGIC_VECTOR(7 downto 0)  
    );  
end decoder3_8;  
  
architecture decoder3_8_arc of decoder3_8 is  
begin  
    dout <= ("10000000") when (din="000") else  
        ("01000000") when (din="001") else  
        ("00100000") when (din="010") else  
        ("00010000") when (din="011") else  
        ("00001000") when (din="100") else  
        ("00000100") when (din="101") else  
        ("00000010") when (din="110") else  
        ("00000001");  
  
end decoder3_8_arc;
```

Construct Larger Decoders

- Decoders with enable inputs can be connected together to form a larger decoder
- The enable input is used as the most significant bit of the selection signal
 - $w=0$: the top decoder is enabled
 - $w=1$: the bottom one is enabled
- In general, enable inputs are a convenient feature for standard components to expand their numbers of inputs and outputs

 


Fig. 4-20 4 × 16 Decoder Constructed with Two 3 × 8 Decoders

Encoder

- A circuit that performs the inverse operation of a decoder
 - Have 2^n (or fewer) input lines and n output lines
 - The output lines generate the binary code of the input positions
- Only one input can be active at any given time
- An extra output may be required to distinguish the cases that $D_0 = 1$ and all inputs are 0

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

Priority Encoder

- An encoder circuit that includes the priority function
- If two or more inputs are equal to 1 at the same time, the input having the highest priority will take precedence
- In the following truth table:
 - $D_3 > D_2 > D_1 > D_0$
 - The X's in output columns represent don't-care conditions
 - The X's in input columns are useful for representing a truth table in condensed form

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

V = 0 :
no valid inputs

Implement a Priority Encoder


		D_2			
		00	01	11	10
D_0	00	X	1	1	1
	01		1	1	1
	11		1	1	1
	10		1	1	1


$$x = D_2 + D_3$$

		D_2			
		00	01	11	10
D_0	00	X	1	1	
	01	1	1	1	
	11	1	1	1	
	10		1	1	

$$y = D_3 + D_1 D'_2$$
 
$$\begin{aligned} x &= D_2 + D_3 \\ y &= D_3 + D_1 D'_2 \\ V &= D_0 + D_1 + D_2 + D_3 \end{aligned}$$






Outline


- Combinational Circuits
- Analysis and Design Procedures
- Binary Adders
- Other Arithmetic Circuits
- Decoders and Encoders
- Multiplexers

Multiplexer

 - A circuit that selects binary information from one of many input lines and directs it to a single output lines
 - Have 2^n input lines and n selection lines
 - Act like an electronic switch (also called a ***data selector***)
- For the following 2-to-1-line multiplexer:
 - $S=0 \rightarrow Y = I_0$; $S=1 \rightarrow Y = I_1$




(a) Logic diagram

 

 (b) Block diagram

4-to-1-Line Multiplexer

- The combinations of S_0 and S_1 control each AND gates
- Part of the multiplexer resembles a decoder
- To construct a multiplexer:
 - Start with an n -to- 2^n decoder
 - Add 2^n input lines, one to each AND gate
 - The outputs of the AND gates are applied to a single OR gate



s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

Quadruple 2-to-1-Line Multiplexer

- Multiplexers can be combined with **common selection inputs** to provide multiple-bit selection logic
- Quadruple 2-to-1-line multiplexer:
 - Four 2-to-1-line multiplexers
 - Each capable of selecting one bit of the 2 4-bit inputs
 - E: enable input
E=1: disable the circuit
(all outputs are 0)

