



# CS230: Digital Logic Design and Computer Architecture

## Lecture 3: Combinational Circuits

<https://www.cse.iitb.ac.in/~biswa/courses/CS230/main.html>

<https://www.cse.iitb.ac.in/~biswa/>



Phones (smart/non-smart)  
on silence plz, Thanks



# Logistics

- Join Piazza now
- Lab-1 will be up soon (mostly on Friday)
- Do come with your queries for Monday's lab.
- Tutorial for selected students on Monday 4:20 PM
  
- Problem set 1 is up. Ungraded, for your practice only
- Detailed course content is at the ASC.
- Email me: [biswa@cse.iitb](mailto:biswa@cse.iitb) and not on [@iitb](#)

# Combinational Circuits

- Combinational logic is often grouped into larger building blocks to build more **complex systems**
- Hides the **unnecessary gate-level details** to emphasize the function of the building block
- Output is only dependent on the input
- We now examine:
  - Decoder
  - Multiplexer
  - Full adder




# Decoder

- “Input pattern detector”
- $n$  inputs and  $2^n$  outputs
- Exactly one of the outputs is 1 and all the rest are 0s
- The output that is logically 1 is the output corresponding to the input pattern that the logic circuit is expected to detect
- Example: 2-to-4 decoder



The complement of a decoder is encoder

$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

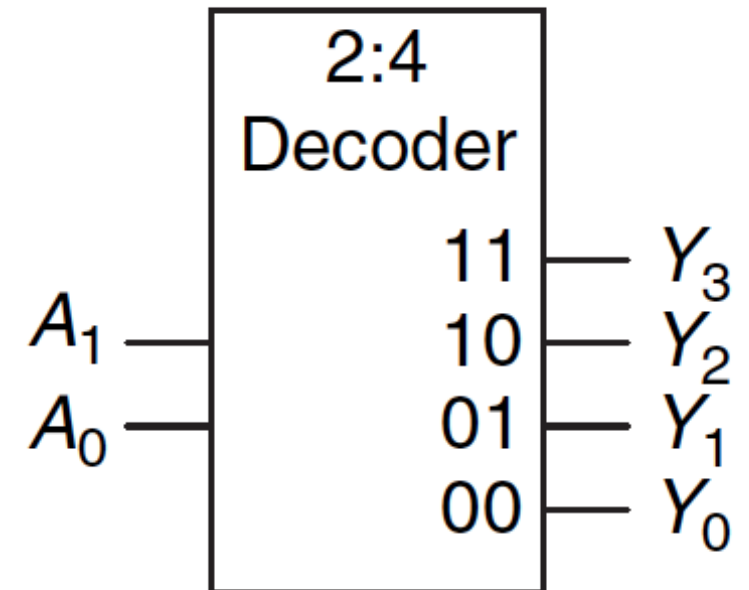

  
# Contd.

- $n$  inputs and  $2^n$  outputs
- Exactly one of the outputs is 1 and all the rest are 0s
- The output that is logically 1 is the output corresponding to the input pattern that the logic circuit is expected to detect
- Mostly decoders have an enable signal. Output is only generated if the enable is high.




- Build a 4x16 decoder using 2x4 decoders (decoder tree)..

<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>EN</i>	<i>minterm</i>
0	0	0	0	1	m0
0	0	0	1	1	m1
0	0	1	0	1	m2
0	0	1	1	1	m3
0	1	0	0	1	m4
0	1	0	1	1	m5
0	1	1	0	1	m6
0	1	1	1	1	m7
1	0	0	0	1	m8
1	0	0	1	1	m9
1	0	1	0	1	m10
1	0	1	1	1	m11
1	1	0	0	1	m12
1	1	0	1	1	m13
1	1	1	0	1	m14
1	1	1	1	1	m15
X	X	X	X	0	0

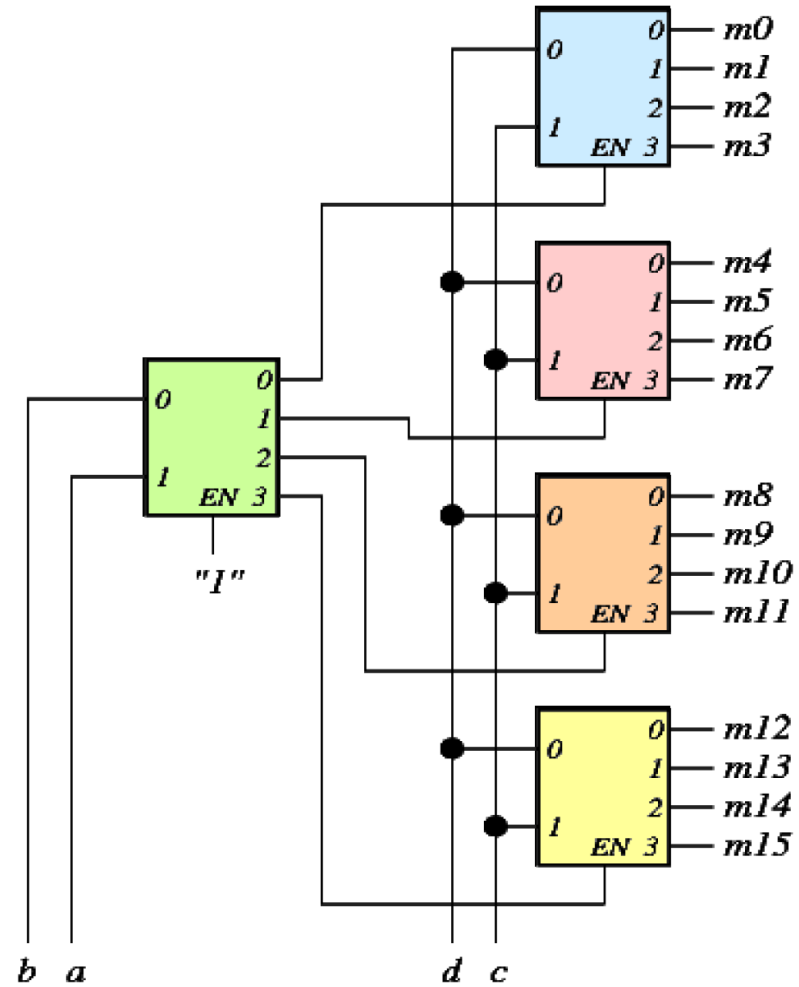
 
# Multiplexer

- Selects one of the  $N$  inputs to connect it to the output
  - based on the value of a  $\log_2 N$ -bit control input called select
- Example: 2-to-1 MUX
- When  $S$  is 0,  $Y$  is  $D_0$  and when  $S$  is 1,  $Y$  is  $D_1$





$S$	$D_1$	$D_0$	$Y$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1




  
## Contd.

- Selects one of the  $N$  inputs to connect it to the output
  - based on the value of a  $\log_2 N$ -bit control input called select
- Example: 2-to-1 MUX




# From 2 to 4:1 MUX

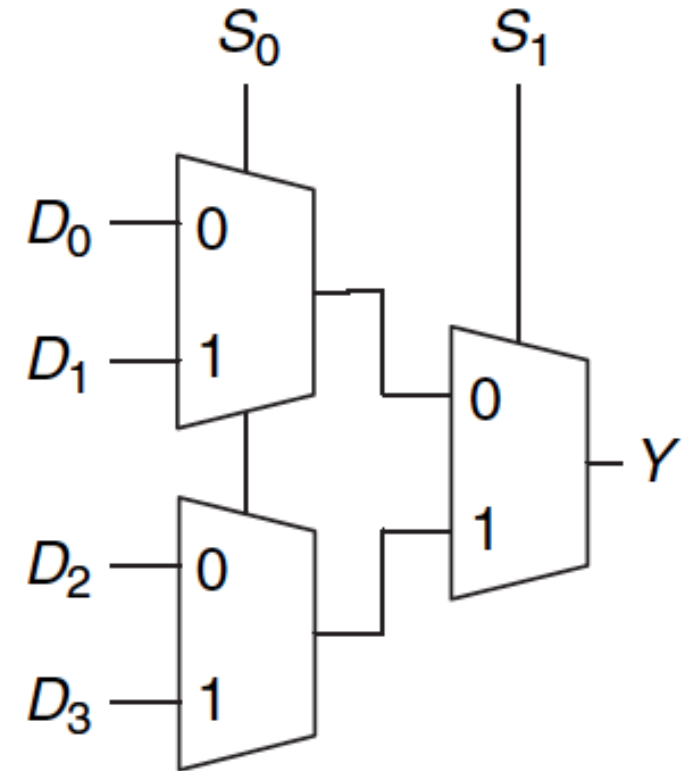 

# Adder


- The most basic arithmetic operation in a digital computer is addition.
- Half Adder is a combination circuit that performs addition of 2 bits.

Inputs		Outputs	
<i>a</i>	<i>b</i>	<i>Carry</i>	<i>Sum</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

$$\begin{aligned} \text{Sum} &= \bar{a}b + a\bar{b} = a \oplus b \\ \text{Carry} &= ab \end{aligned}$$

## Half adder

 

$$Sum = \bar{a}b + a\bar{b} = a \oplus b$$
$$Carry = ab$$

- Half adders cannot accept a carry input and hence it is not possible to cascade them to construct an  $n$ -bit binary adder.

# Full adder

- Full Adder is a combinational circuit that forms the arithmetic sum of three input bits. It is described by the following truth table:


Inputs			Outputs	
<i>c</i>	<i>b</i>	<i>a</i>	<i>C<sub>out</sub></i>	<i>Sum</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1




$$\begin{aligned} \text{Sum} &= \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc = a \oplus b \oplus c \\ \text{C}_{out} &= ab + ac + bc = ab + c(a + b) \end{aligned}$$
 
# Implementation

$$\text{Sum} = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc = a \oplus b \oplus c$$
$$C_{out} = ab + ac + bc = ab + c(a + b)$$




Full Adder at bit  $i$


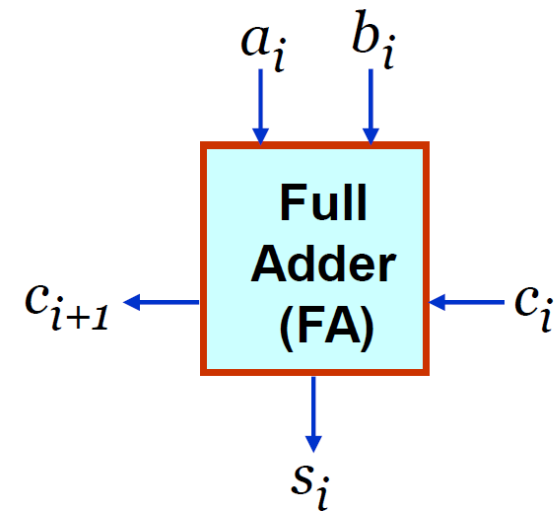





# Ripple Carry Adder

 

# Comparator (Equality Checker)

  

# ALU (Arithmetic Logic Unit)

 

**ALU symbol**

**ALU operations**


$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND $\bar{B}$
101	A OR $\bar{B}$
110	A - B
111	SLT


A photograph of a white ceramic coffee cup filled with dark coffee, sitting on a matching saucer. The cup and saucer are placed on a light-colored surface, possibly a windowsill, with a dark background behind them. The word "PAUSE" is written in white, uppercase letters across the center of the cup. The lighting is soft, creating a calm and contemplative atmosphere.

PAUSE
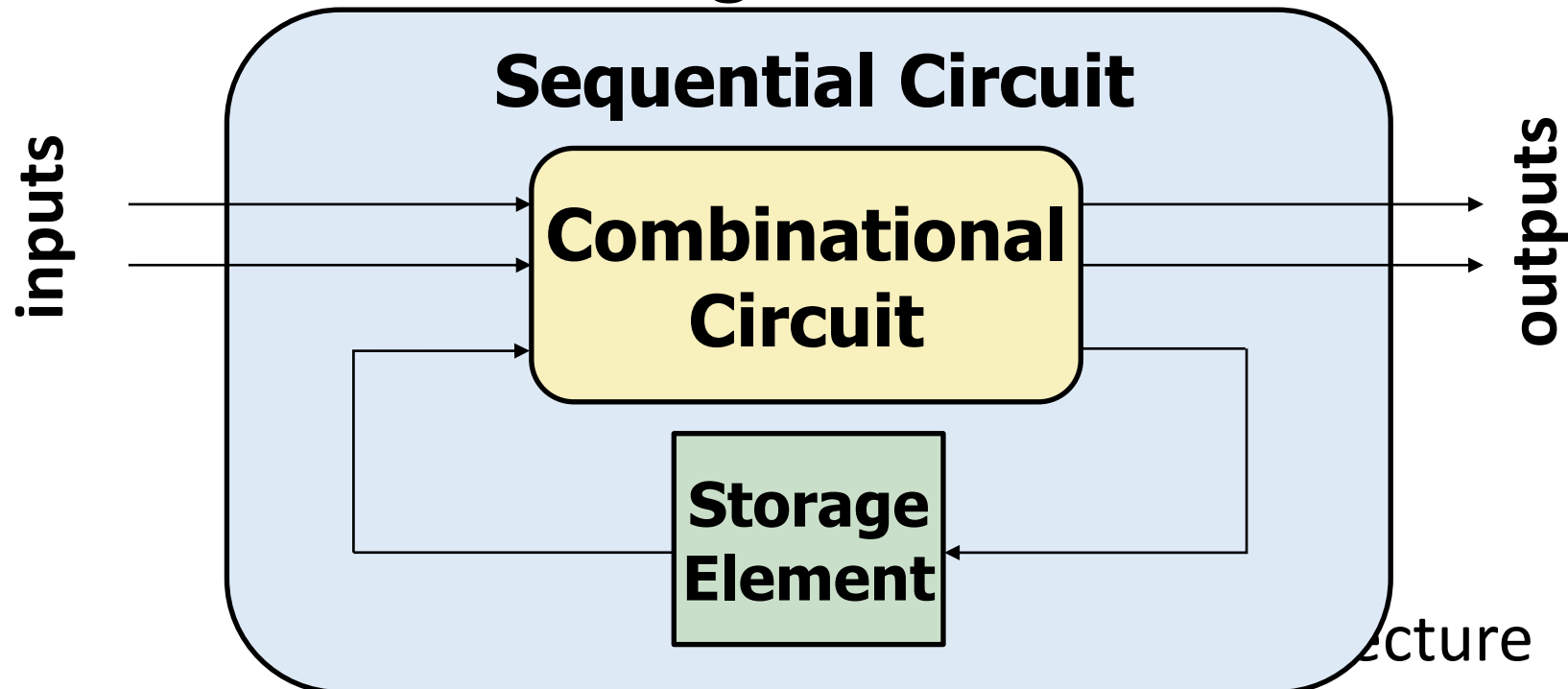
# Sequential Circuit

- Combinational circuit output depends **only** on **current** input
- We want circuits that produce output depending on **current** and **past** input values – circuits with **memory**
- How can we design a circuit that **stores information**?



 

# Textbook Reading

Chapter 2.8 H&H



# Coffee points:

- Atharva 210070014





আপনার দিনটি শুভ হোক