



CS230: Digital Logic Design and Computer Architecture

Lecture 4: Sequential Circuits

<https://www.cse.iitb.ac.in/~biswa/courses/CS230/main.html>

<https://www.cse.iitb.ac.in/~biswa/>



Phones (smart/non-smart)
on silence plz, Thanks




Logistics

- Join Piazza now, plz
- Lab-1 will be up after today's lecture
- Do come with your queries for Monday's lab.
- Tutorial for selected students on Monday 4:20 PM, Try the problem set-I before coming to tutorial


Quiz-1 on January 27

Sequential Circuit

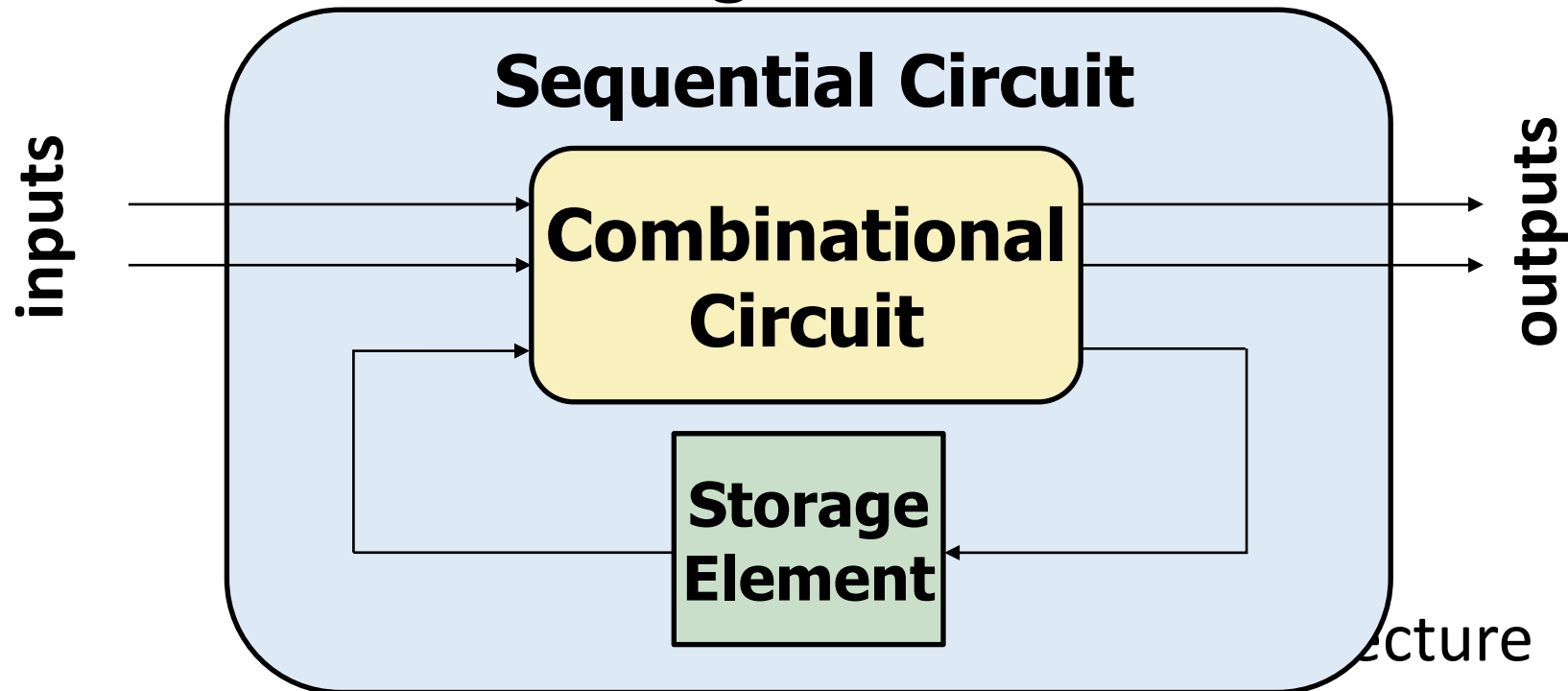
- Combinational circuit output depends **only** on **current** input
- We want circuits that produce output depending on **current** and **past** input values – circuits with **memory**
- How can we design a circuit that **stores information**?



The base for any storage

 

(a)

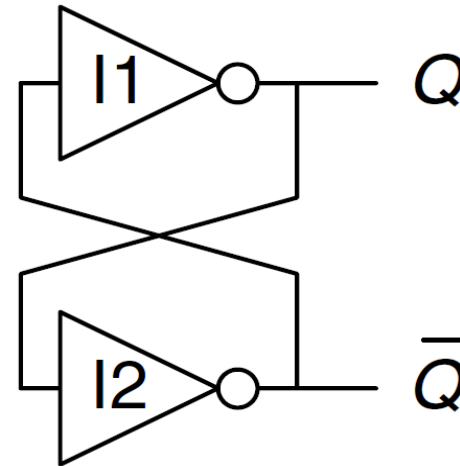


(b)

If Q is zero then Q complement is 1. Note that the circuit has no inputs 😊

The Clock as some need it

- Clock signals are usually periodic.

 

- Duty cycle = ON Time / Clock Period
- Frequency = 1/Time Period
 - Units are in Hz

Clock is driven by the slowest combinational circuit/path.
Clock is responsible for triggering a state change



Clock

Logic beat (like heart beat) oscillates between high and low voltage but at a constant frequency

Clock and Storage Elements



Storage elements are affected only at the arrival of a clock pulse.



Storage elements are usually called as a latch/flip-flop.



They maintain a binary state until directed by a clock pulse.

S-R Latch

- Cross-coupled NOR/NAND **gates**
 - Data is stored at **Q** (inverse at **Q'**)
 - **S** and **R** are control inputs
 - **S** = Set, $Q=1 \rightarrow S=1, Q=0; S=0$
 - **R** = Reset





S-R Latch

Three inputs: Set, Reset, and a proxy clock

Circuit works only when the proxy clock is ON


S=Set

R=Reset

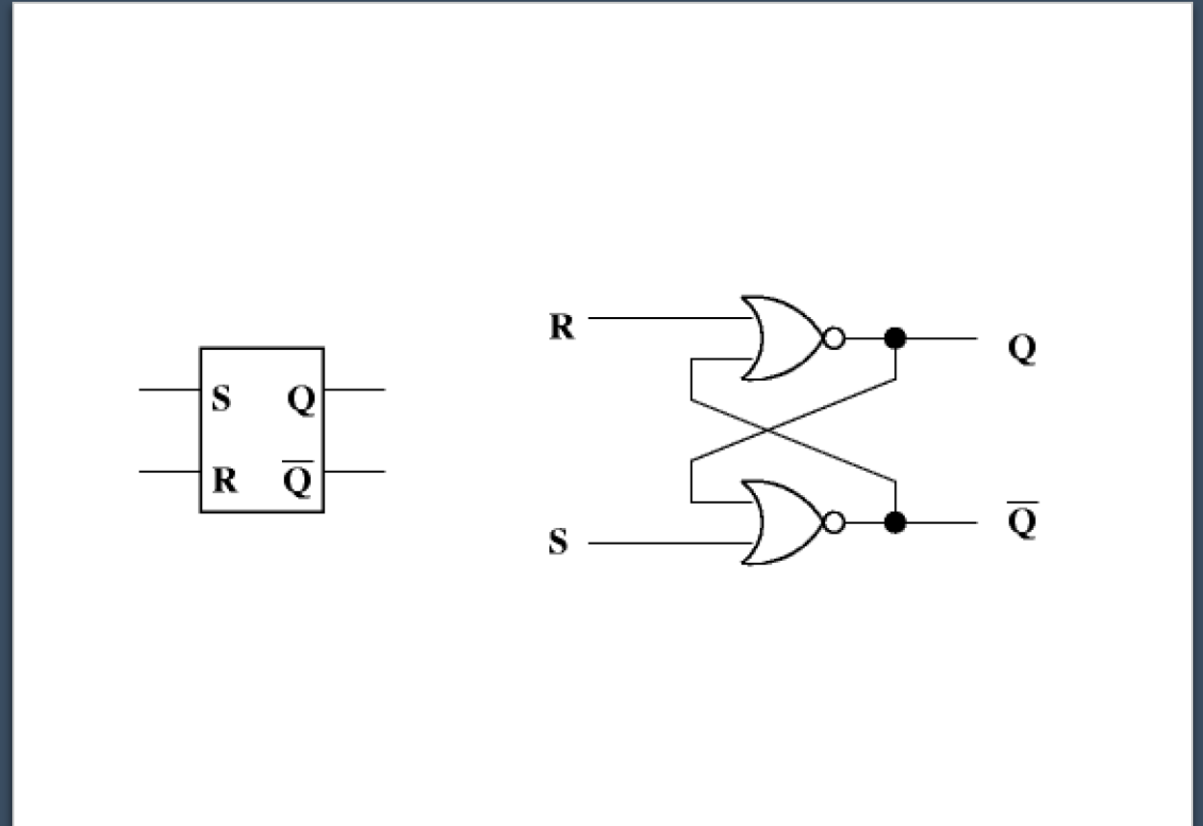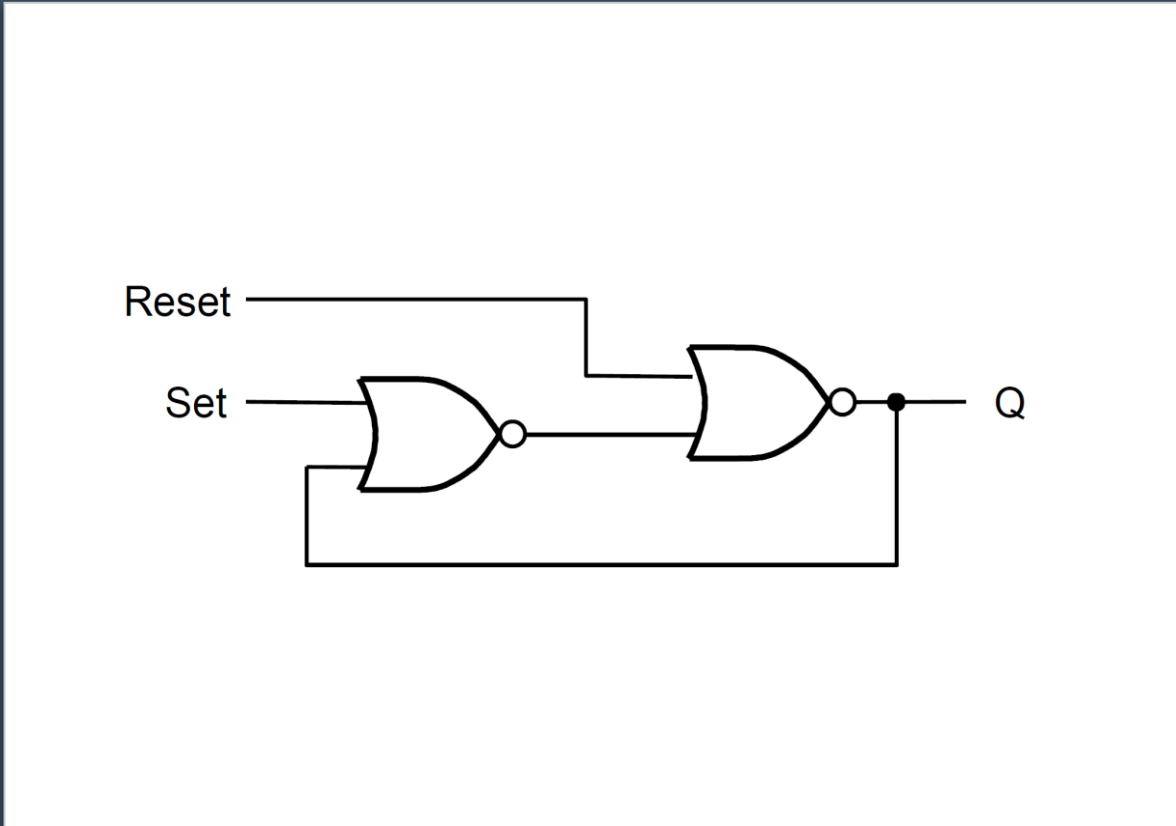

Contd.

 Given the current state and inputs to a latch, what is the next state. Typically, symbols Q , Q_{n-1} , Q^t , etc. are used to denote the current state, and correspondingly, Q^* , Q_n , Q^{t+1} , etc. denote the next state.




S	R	Q^*
0	0	Q
0	1	0
1	0	1
1	1	<i>Undefined (0 0)</i>

NAND gates


- Cross-coupled **NAND gates**

- Data is stored at **Q** (inverse at **Q'**)
- **S** and **R** are control inputs
 - In *quiescent (idle) state*, both **S** and **R** are held at **1**
 - **S (set)**: drive **S** to 0 (keeping **R** at 1) to change **Q** to 1
 - **R (reset)**: drive **R** to 0 (keeping **S** at 1) to change **Q** to 0

 - **S** and **R** should never **both** be 0 at the same time



Input		Output
R	S	Q
1	1	Q_{prev}
1	0	1
0	1	0
0	0	Forbidden

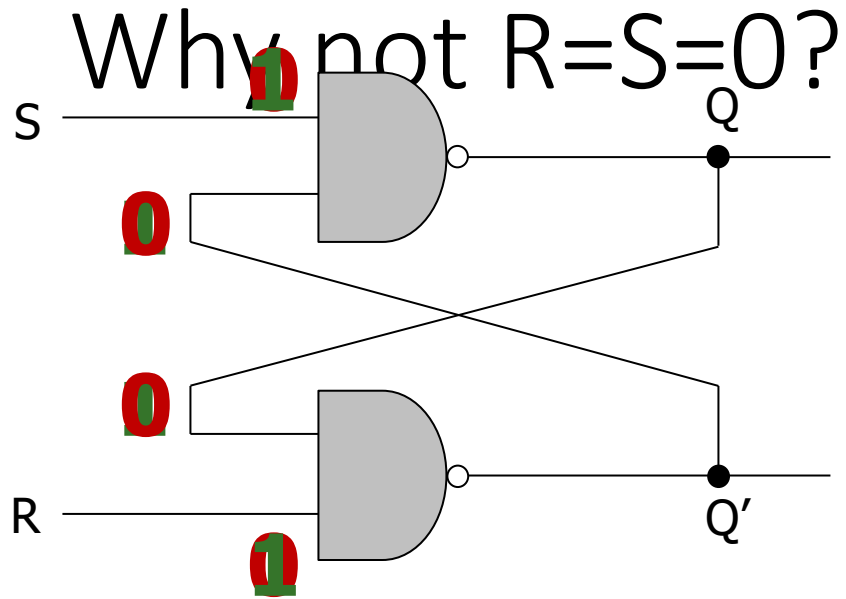


Input		Output
R	S	Q
1	1	Q_{prev}
1	0	1
0	1	0
0	0	Forbidden

 1. If $R=S=0$, Q and Q' will both settle to 1, which **breaks** our invariant that $Q = \neg Q'$
2. If S and R transition back to 1 at the same time, Q and Q' begin to oscillate between 1 and 0 because their final values depend on each other (**metastability**)
 - This eventually settles depending on **variation in the circuits**

Gated D-latch

- How do we **guarantee** correct operation of an S-R Latch?
 - Add two more NAND gates!



Input		Output
WE	D	Q
0	0	Q_{prev}
0	1	Q_{prev}
1	0	0
1	1	1

- **Q** takes the value of **D**, when **write enable (WE)** is set to 1
- **S** and **R** can never be 0 at the same time!




Why are latches not preferred? Coffee points++

The inputs should not change while the gate signal is asserted (otherwise there are multiple state changes which can lead to problems in a circuit).

One Solution


- What if we change our states only on clock edge and call me edge-triggered

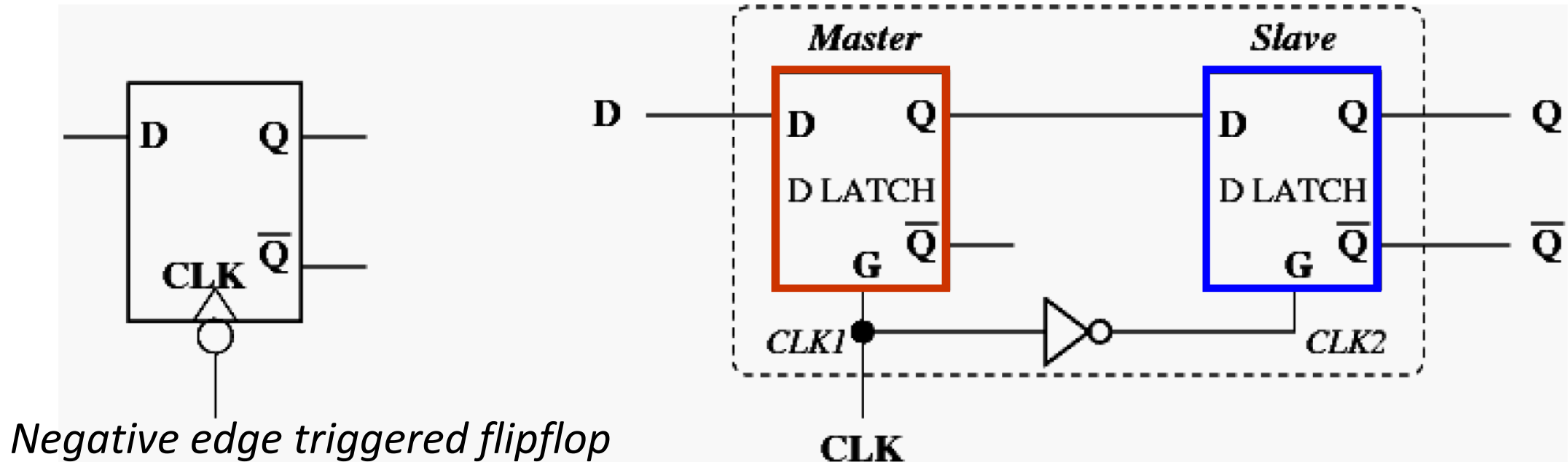Edge Triggering Master-slave D Flip-flop with two latches



At a given time, only one latch is alive (either master or slave)


Level/Edge Triggered

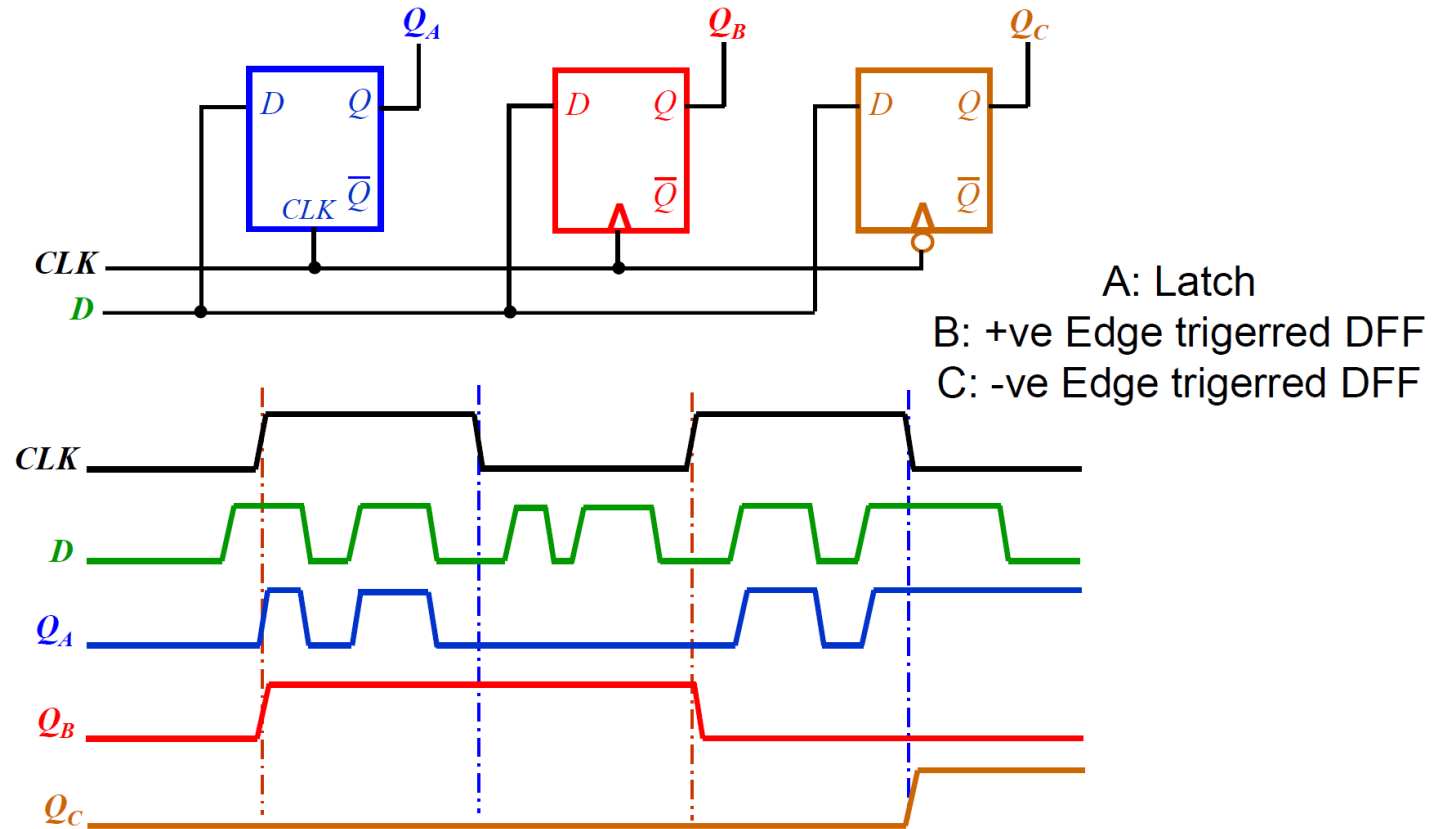

Summary



 
Gates are building blocks of combinational circuits



Latches are
.....
sequential circuits



Latches are built from gates

 


Flip-flops are built from latches

Register

How can we use D latches to store **more** data?

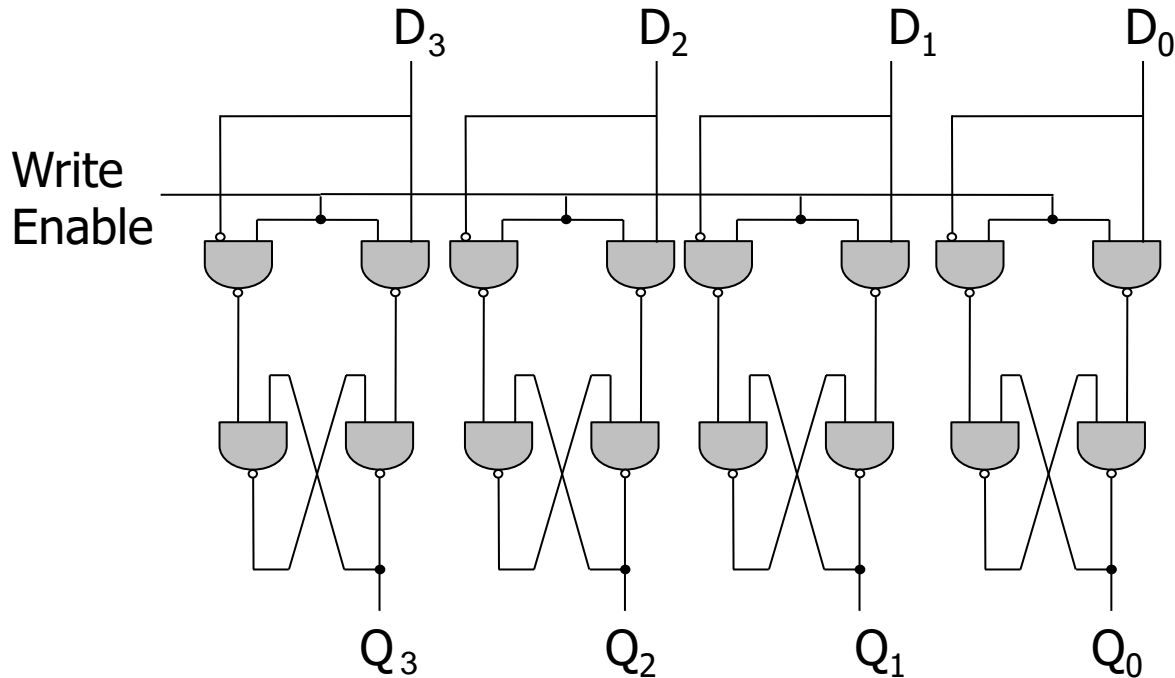- Use **more** D latches!
- A single WE signal for all latches for simultaneous writes




Here we have a **register**, or a structure that stores more than one bit and can be read from and written to

This **register** holds 4 bits, and its data is referenced as $Q[3:0]$

Register


How can we use D latches to store **more** data?

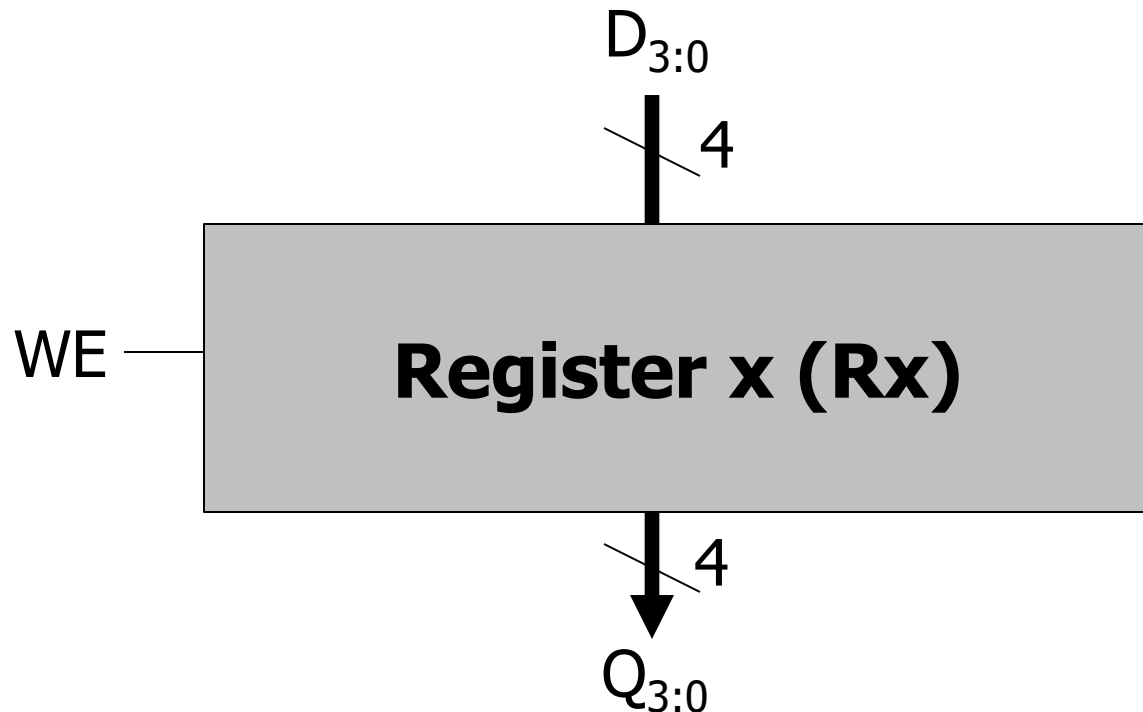- Use **more** D latches!
- A single WE signal for all latches for simultaneous writes



Here we have a **register**, or a structure that stores more than one bit and can be read from and written to

 This **register** holds 4 bits, and its data is referenced as Q[3:0]





Sequential circuit 101 again

Combination of latches/flip-flops and combinational elements (gates).

Flip-flops need a clock

An Example
(Let's try it)

 

 


Present state		Input x	Next state		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0


$$A(t+1) = Ax + Bx, \quad B(t+1) = A'x, \quad y = Ax' + Bx'$$

State Table

State Diagram

 
x/y where x is input and y is output after the transition





Try it for a binary counter 😊

Lab-1 coming up



World of State machines (FSMs) Moore and Mealy Machines

Computer Architecture

Moore vs Mealy



Moore machine: Output depends on the current state




Mealy machine: Output depends on the current state and inputs


Odd Parity Checker

- Serial input string
 - OUT=1 if odd # of 1s in input
 - OUT=0 if even # of 1s in input
- Let's do this for Moore and Mealy

Moore

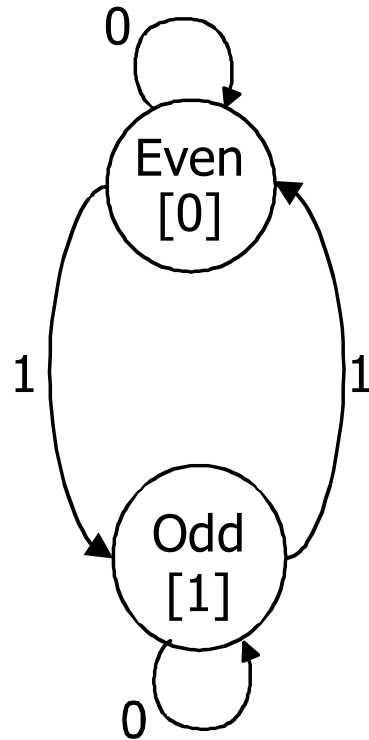

Mealy

 

State Transitions

Output changes only when the state changes
Appears after the state transition takes place
outputs change at clock edge

Even = 0
 Odd = 1

Moore

Present State	Input	Next State	Present Output
Even	0	Even	0
Even	1	Odd	0
Odd	0	Odd	1
Odd	1	Even	1

Output changes when the state and input changes
Appears before the state transition is completed
React faster to inputs — don't wait for clock


Mealy

Present State	Input	Next State	Present Output
Even	0	Even	0
Even	1	Odd	1
Odd	0	Odd	1
Odd	1	Even	0




Try on your own

01/10 detector: Moore Machine

 

reset	input	current state	next state	current output
1	—	—	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	D	0
0	0	C	E	0
0	1	C	C	0
0	0	D	E	1
0	1	D	C	1
0	0	E	B	1
0	1	E	D	1

01/10 detector: Mealy Machine

 

reset	input	current state	next state	current output
1	—	—	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	C	1
0	0	C	B	1
0	1	C	C	0

Textbook Reading

H&H, 3.2 and 3.4

Coffee Credits

Anshika 210050014



இந்த நாள் இனிய நாளாகட்டும்